
AUDIO AMPLIFIER

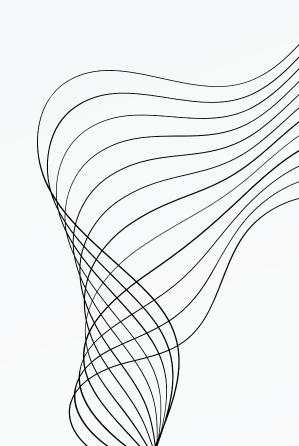PRIYA MANDOT(2022102053), SAMKIT JAIN(2022102062)



CONTENT

01

IINTRODUCTION

02

MICROPHONE

03

PRE AMP 1: DIFFERENTIAL AMPLIFIER

04

PRE AMP 2: CE AMPLIFIER

05

PASSIVE BANDPASS FILTER

06

POWER AMPLIFIER

07

FINAL RESULT




INTRODUCTION




An essential component in audio systems, the Audio Amplifier serves as an analog circuit primarily tasked with amplifying audio signals. Its primary function is to boost the power of an audio signal, typically sourced from a microphone, to a level suitable for playback through a speaker.

Breadboard

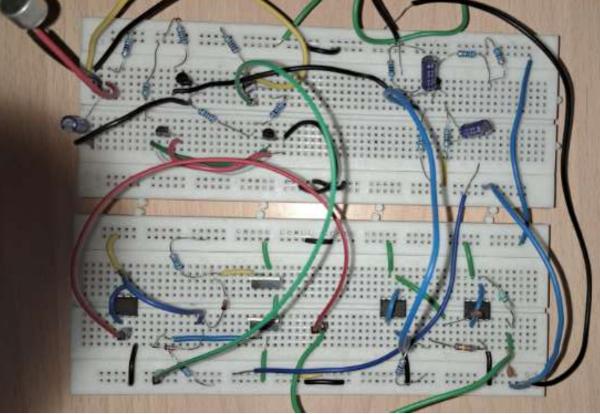

FULL CIRCUIT SIMULATION

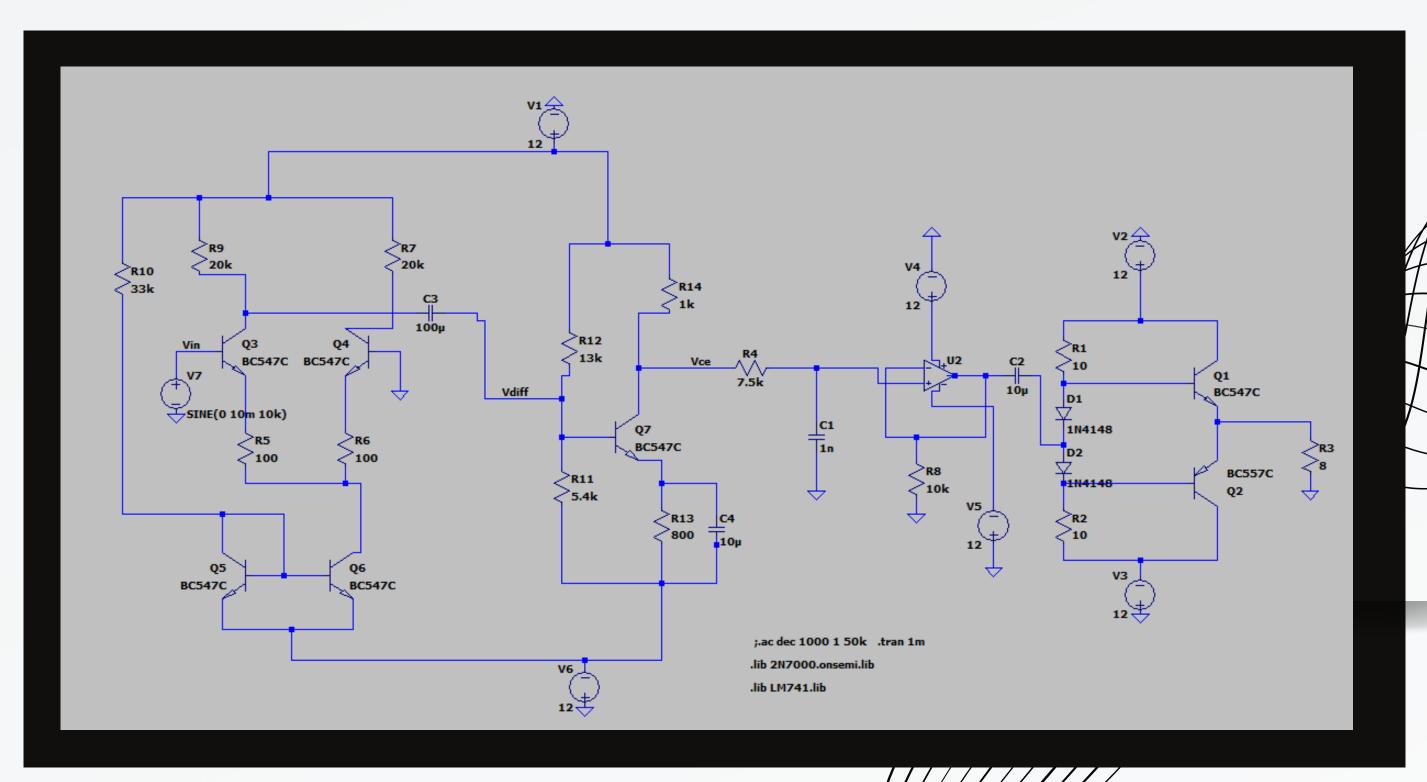

STAGES

1) Pre Amplifier

Focuses on amplifying the amplitude (voltage) of the input from the mic. It involves cascading multiple voltage amplifiers to achieve the necessary gain.


2) Filter

Plays a crucial role in removing frequencies outside the desired range (20 Hz- 20000 Hz).

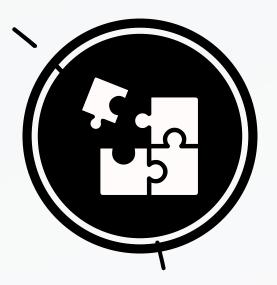3) Power Amplifier

Increasing the current directed to the output load, ensuring that the appropriate power is delivered to the speaker.





MICROPHONE

Circuit +12 V R > 10K C TO Pric- Amp

• A microphone is an essential input device used to convert sound waves into electric signals for various applications, such as inputting audio into computers. It captures sound by transforming sound waves into electrical signals, which can be either digital or analog.


 Here the resistor is used to limit current and the capacitor is responsible for amplifier gain which you can connect with this circuit to amplify the signals. The capacitor also blocks any DC signal, allowing a small AC input to flow to the circuit.

Breadboard




PRE AMP 1: DIFFERENTIAL AMPIFIER

Circuit

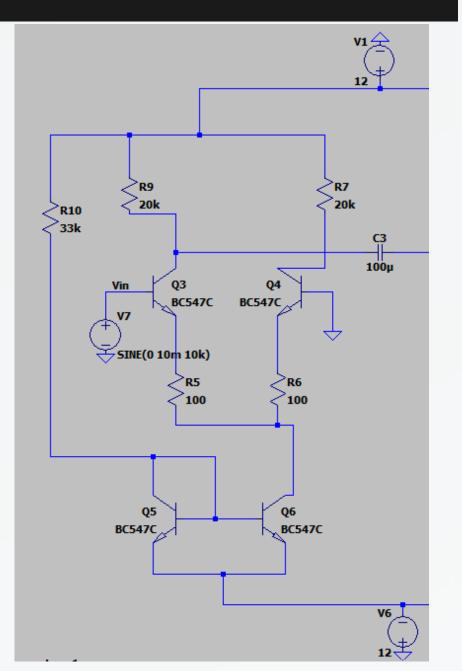


- Differential amplifier consists of two transistors with same emitter and collector currents.
- Designed to cancel out common-mode voltage, providing difference as output.
- Grounding one transistor's base/gate while applying input to the other removes common noise, amplifying input signal.
- Emitter/source ideally connected to constant current source for pull-down load.
- Current mirror used to create adjustable current source for pull-down load.
- Capacitor at output reduces DC offset.
- Resistors are added at the emitter of the Diff amp to increase the range of differential input.

Breadboard

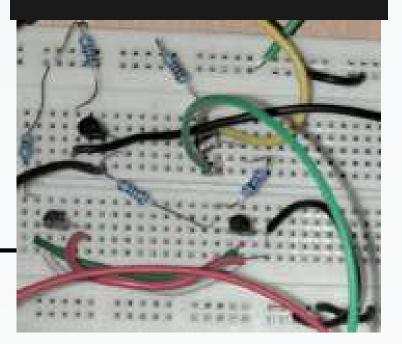


CURRENT MIRROR

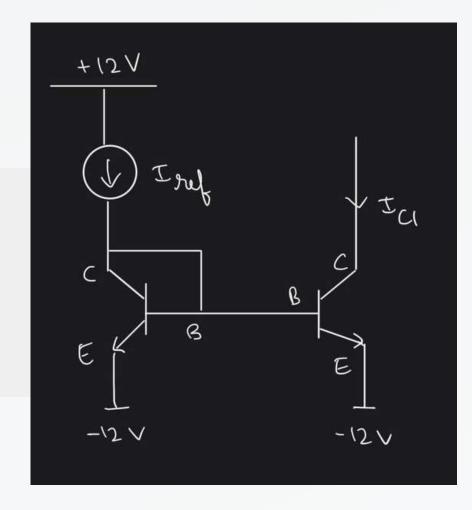
Used to provide bias currents and active loads to circuits. It is used to model a more realistic current source (since ideal current sources do not exist) to provide a constant current at the emitters (le) of the BJT. As a result, le becomes independent of the base resistor and the current gain of the BJT.




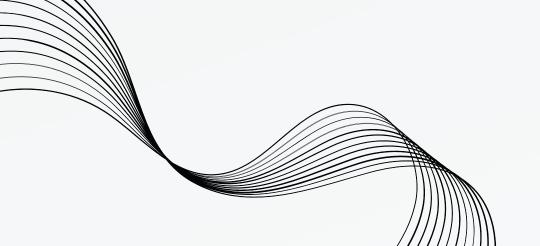Assuming negligible lb: we get Ic approximately equal to Iref and thus Iref/2 applied at the emitters of the Diff amp




ANALYSIS- SMALL SIGNAL

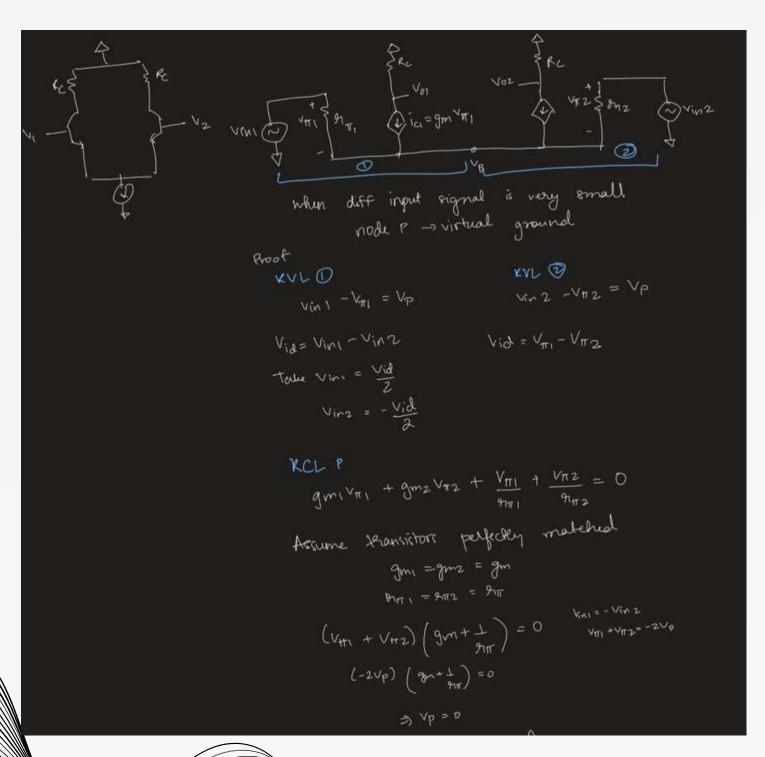

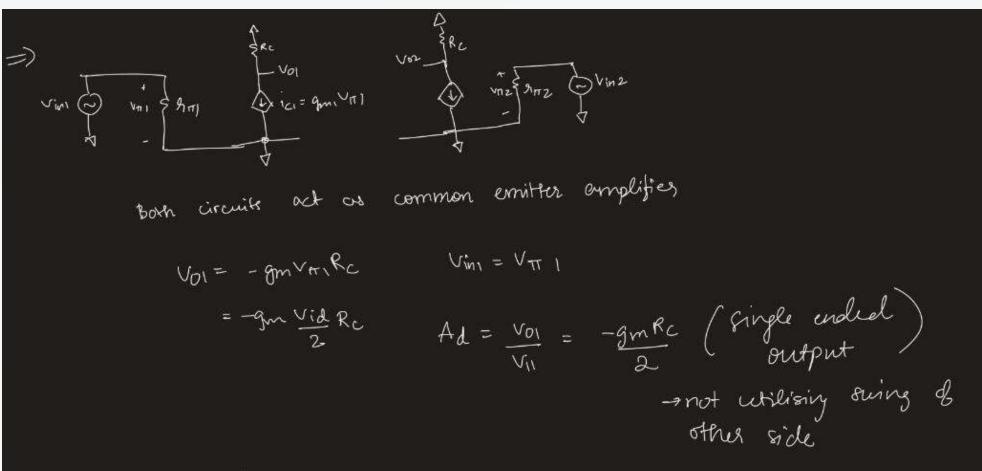


ANALYSIS- CMRR

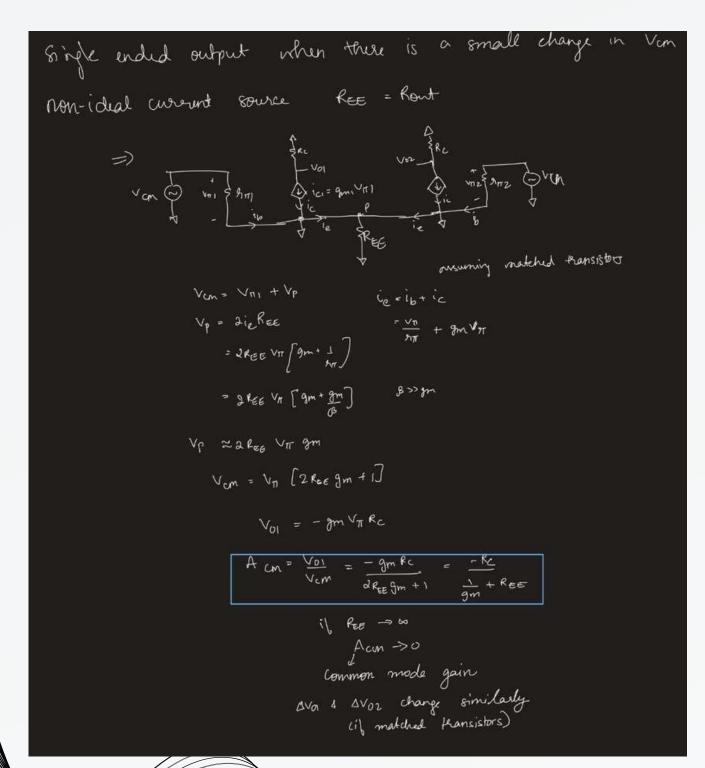


SIMULATIONS

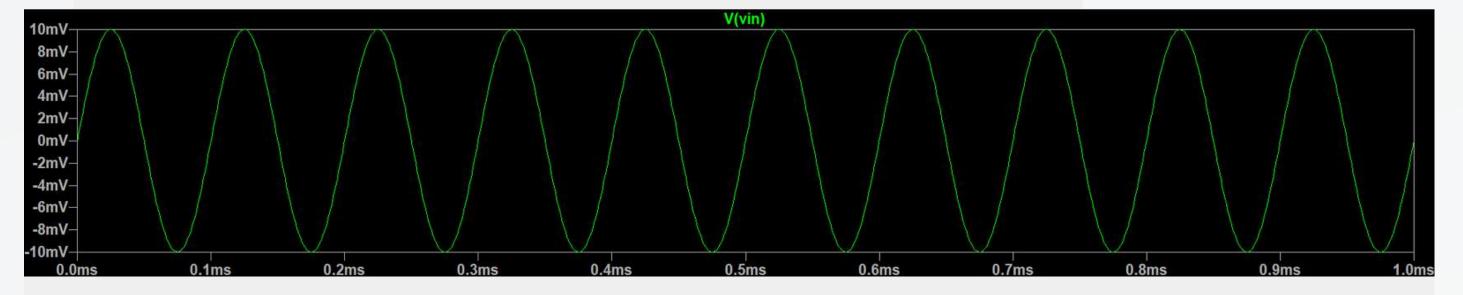
Input - a sine wave of amplitude 10 mV and frequency 10kHz



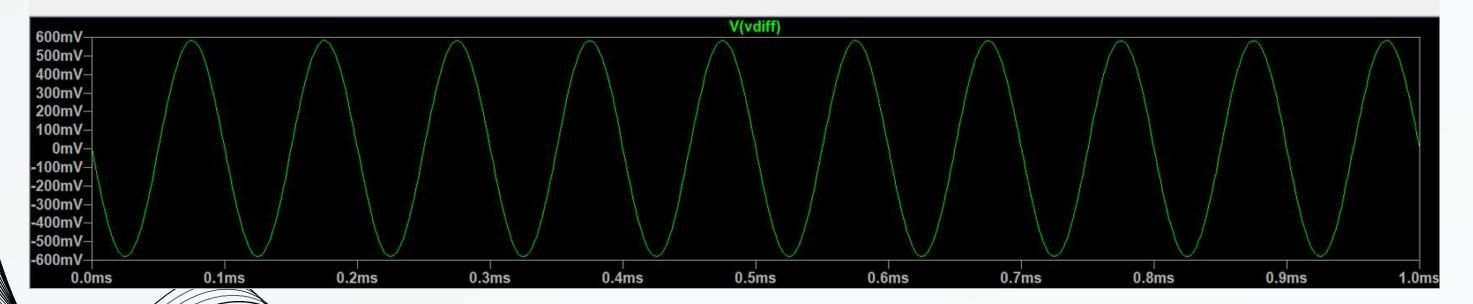Output - Single ended different output. Phase shifted by 180 degrees and a gain of 600/10 = 60




HARDWARE

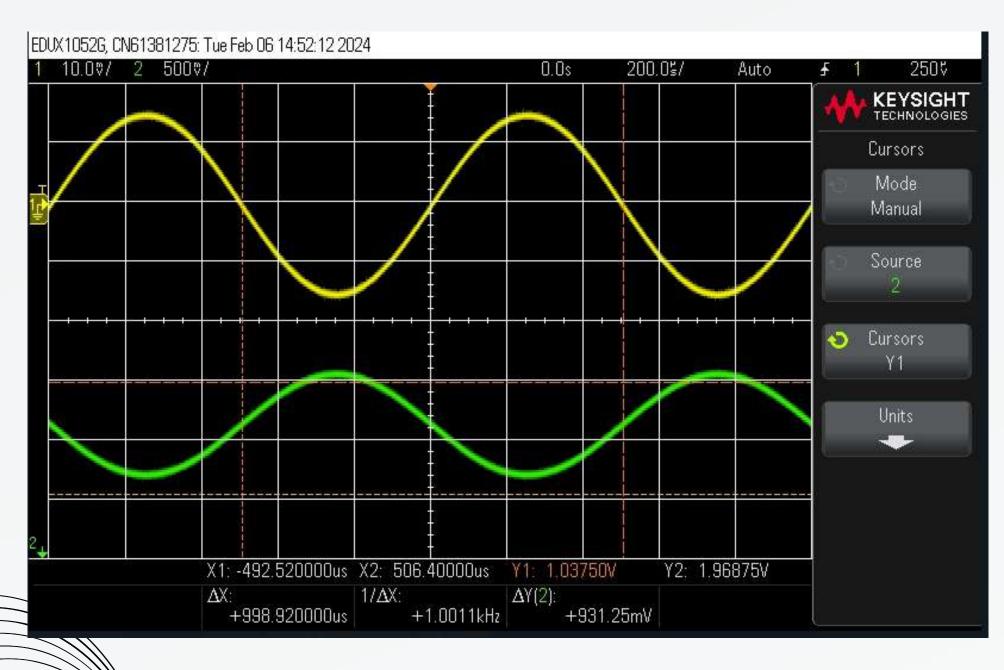


For an input waveform of voltage 30mV we observe an output of 930mV which is a gain of approximately 31.

PRE AMP 2: CE AMPLIFIER


Circuit

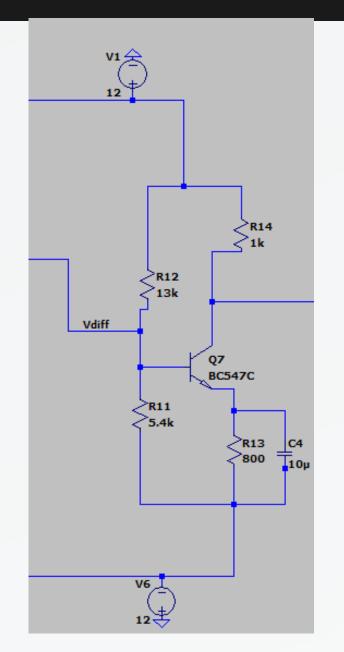


- The common emitter (CE) amplifier is utilized to further amplify the output of the differential amplifier by biasing it to the Linear region
- In this configuration, the emitter resistor (RE) is essential for stabilizing the transistor's operating point.
- Without RE, the emitter voltage directly reflects the negative supply voltage (VEE), leading to a high threshold for transistor activation.
- Including RE ensures a sufficient potential drop for the transistor to remain in its active region.
- It's important to note a 180-degree phase shift between input and output signals in the CE amplifier: an increase in input results in an increase in collector current (Ic) and a decrease in output voltage (Vout).

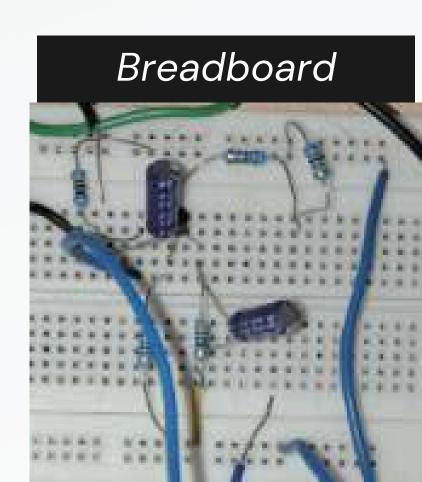


DESIGN

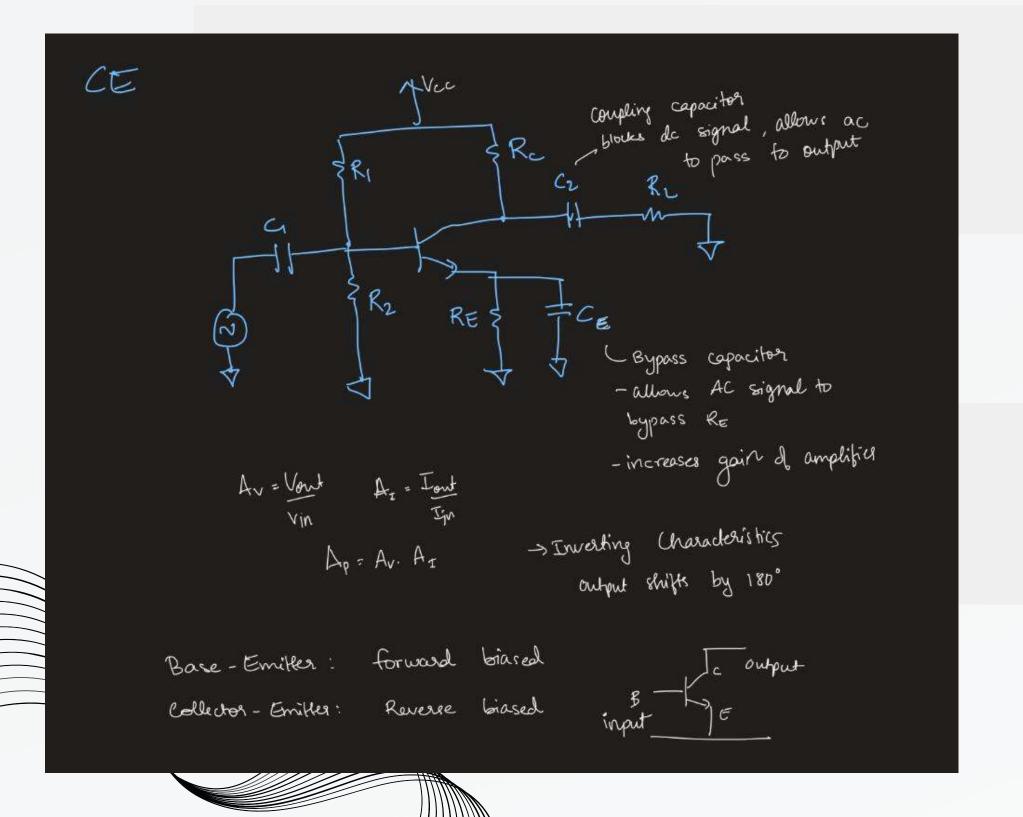

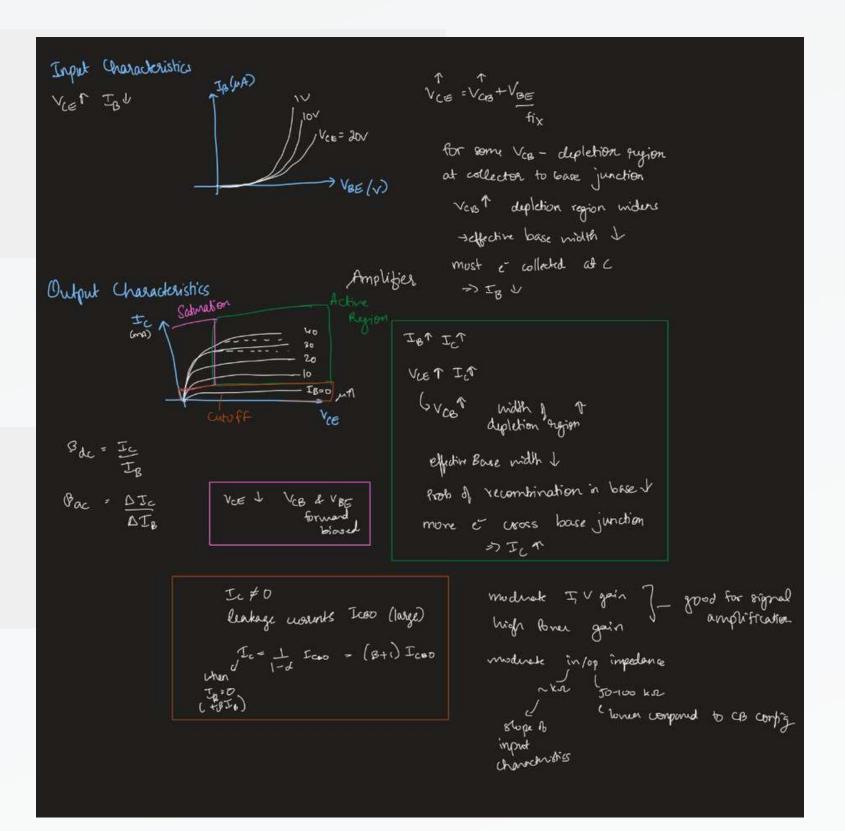


ANALYSIS - SMALL SIGNAL

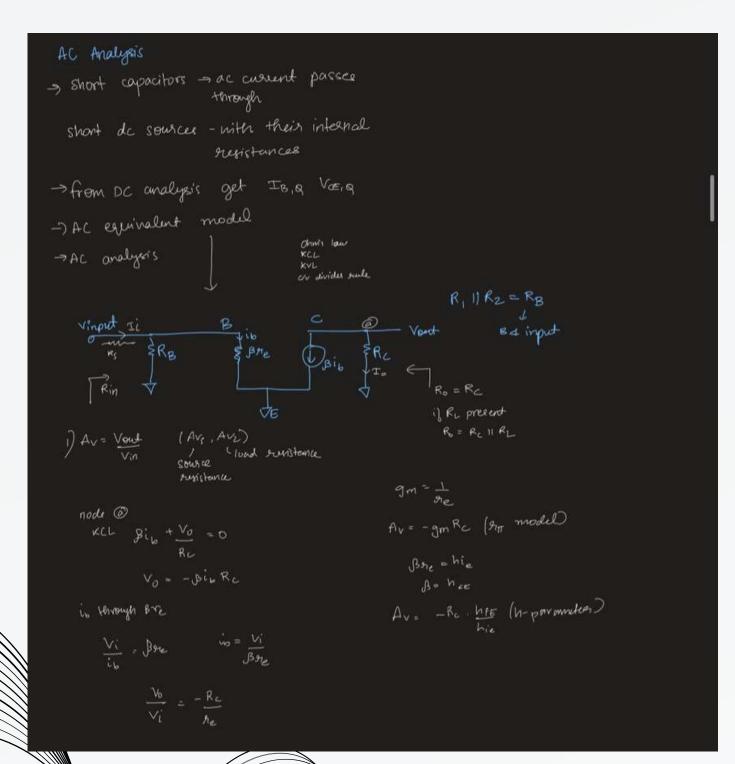

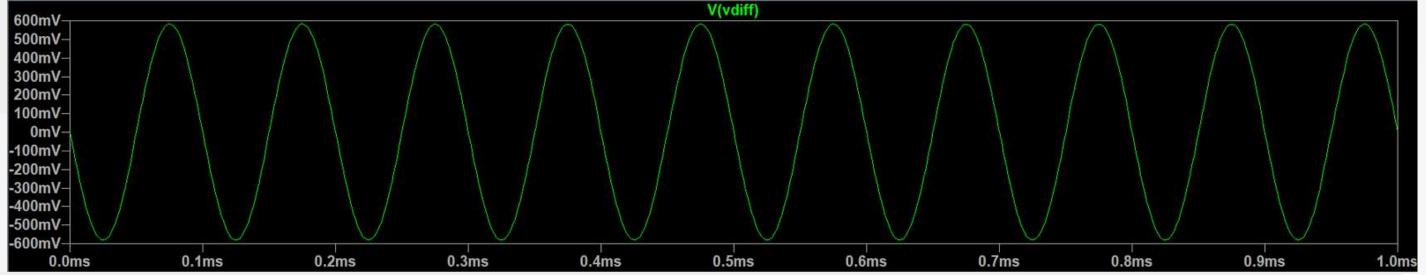
2)
$$A_{\pm}$$
 $T_{0} = -\beta i_{b}$
 $T_{0} = -\beta i_{b}$
 $T_{0} = R_{c}$
 $T_{$

SIMULATIONS


Input - Single ended differential output of 600 mV



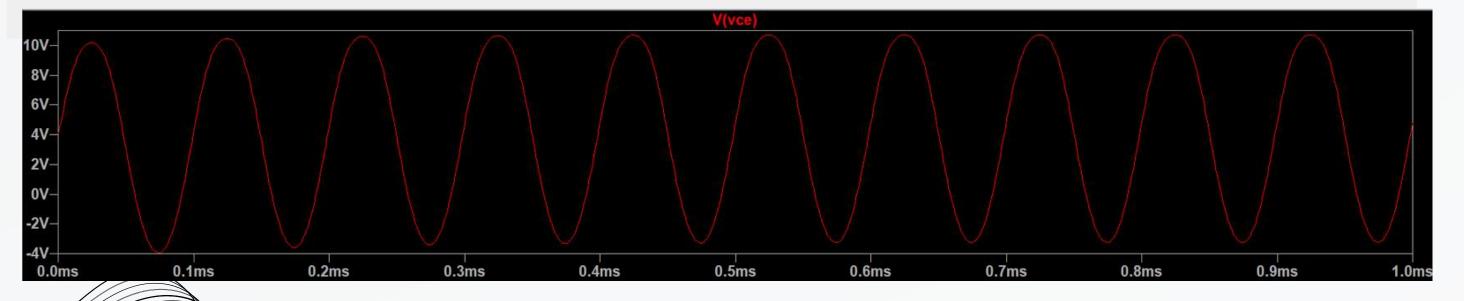Output - Phase shifted but now in phase with input. 6 V output implying CE gain of 10 and a total pre ampifier gain of 600



HARDWARE

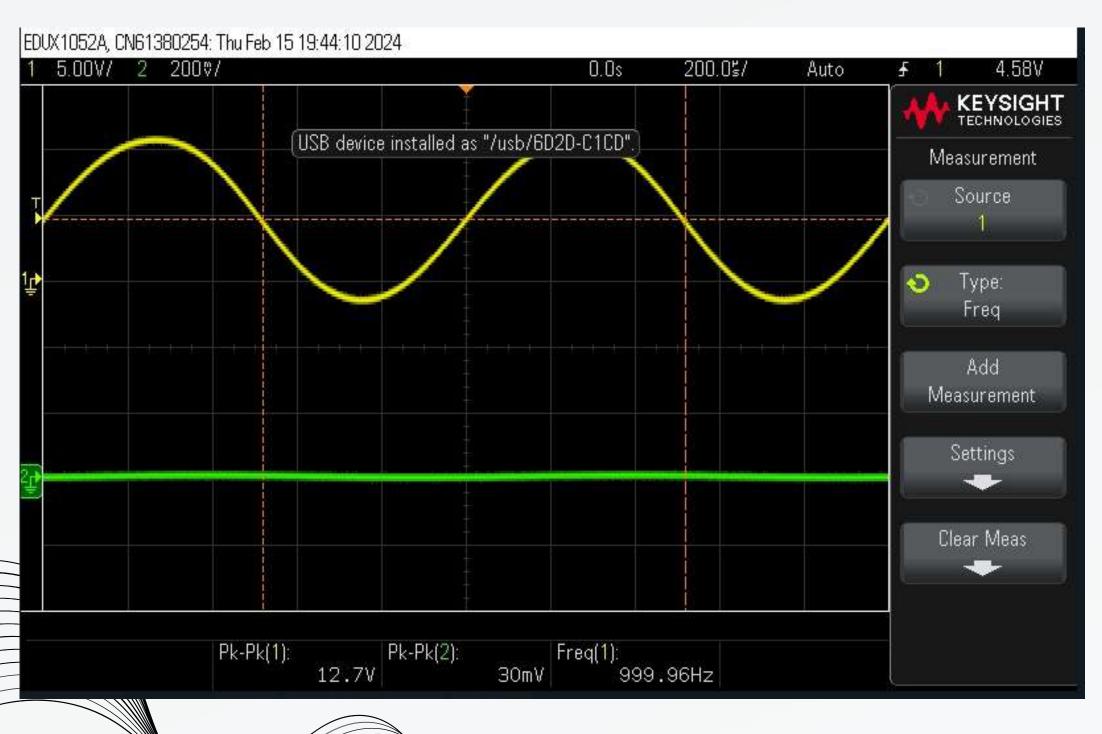


For an input of 30mV into the Differential Amplifier an output of 12.7V is observed at the CE amplifier (Pre-Amp 2). This is an approximate gain of 423.

PASSIVE BANDPASS FILTER

C1 10n R1 333k V2 11 11 11 11 11 11 11 11 11

A filter is used to cut-out the frequencies outside the hearing range of a human, i.e., the frequencies between 20Hz and 20kHz. This is done using passive R and C components.

Breadboard

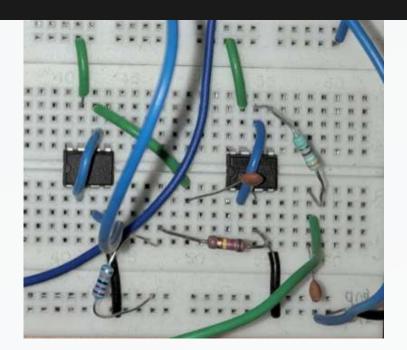


CALCULATIONS

For a passive RC filter, the cut-off frequency is calculated using the expression: $fc=1/2\pi RC$

An op-amp buffer is added between the HPF and the LPF to prevent any issues related loading effects


AC ANALYSIS

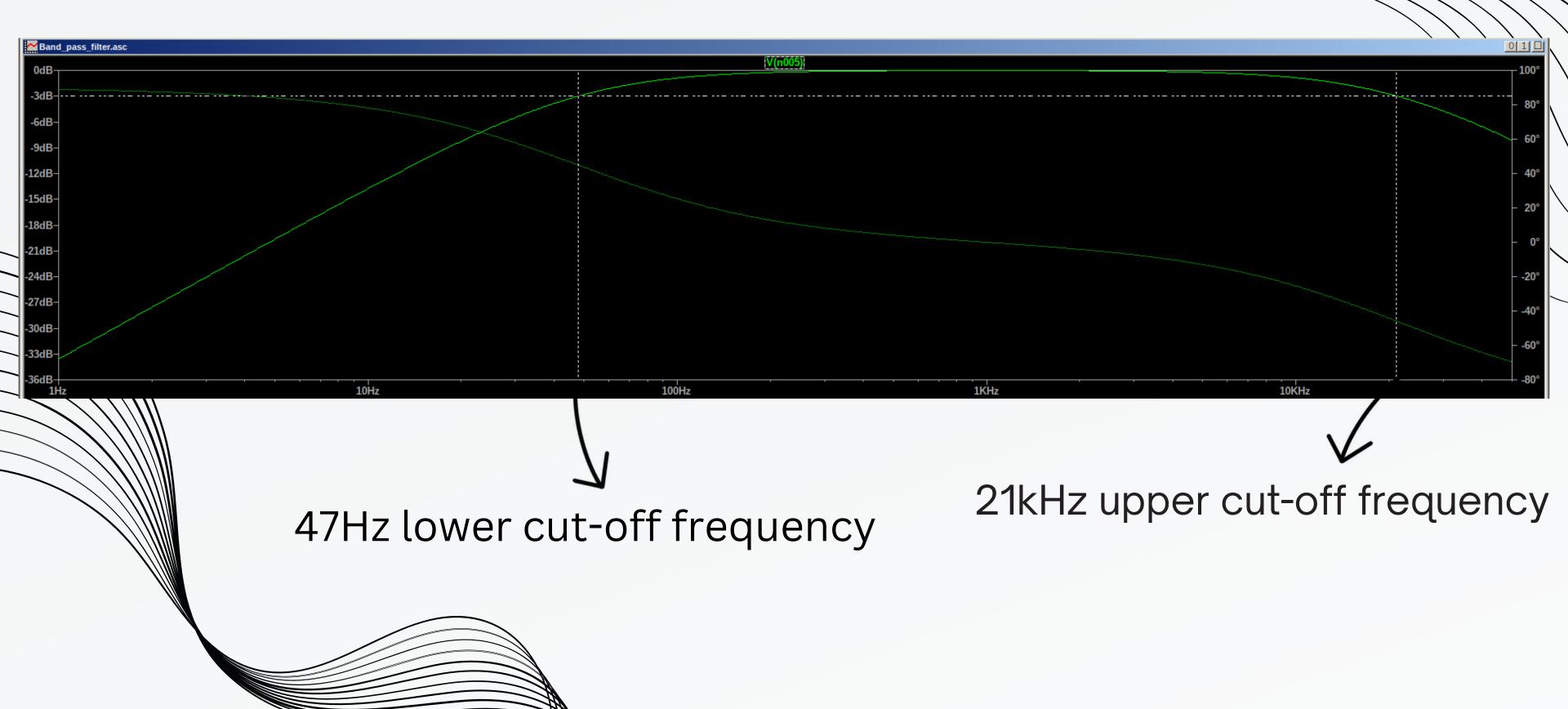

HARDWARE READINGS



ATTENUATION OF FREQUENCIES

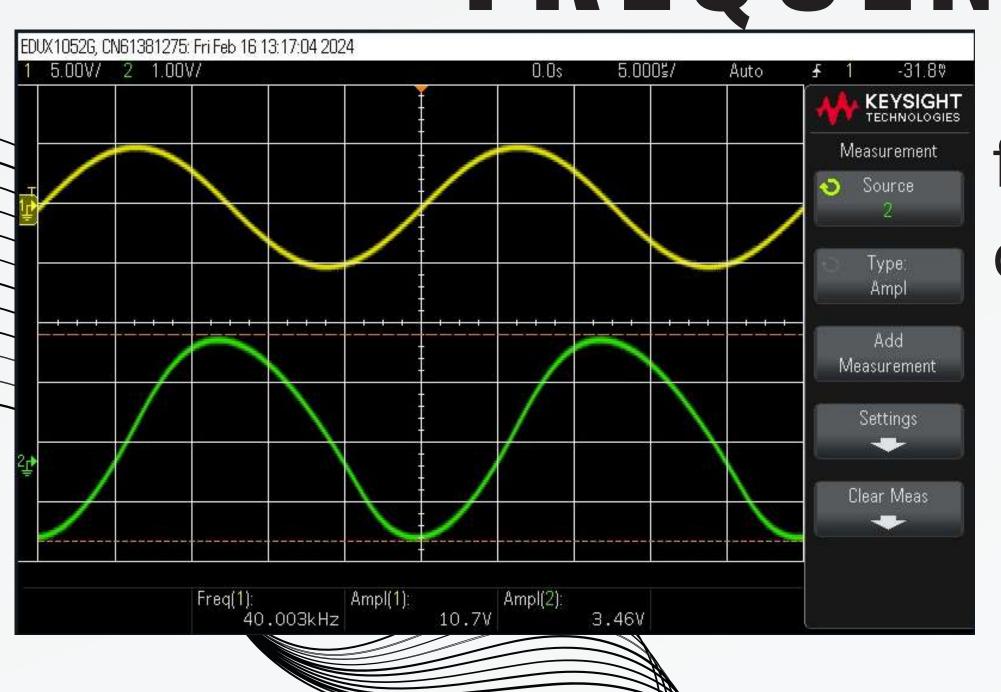

Since the signal frequency is beyond the cut-off frequency of the filter, we observe that there is major attenuation from 10.7V to 3.46V for the signal of frequency 40kHz


POWER-AMP

Simulation BC547C D1 1N4148 D2 BC557C 1N4148 **R2**

A power amplifier is used to increase the power output of the amplifier, so as to run the speaker. The power amplifier increases the current for the same voltage waveform.

This results in an increased power output at the load.


Breadboard

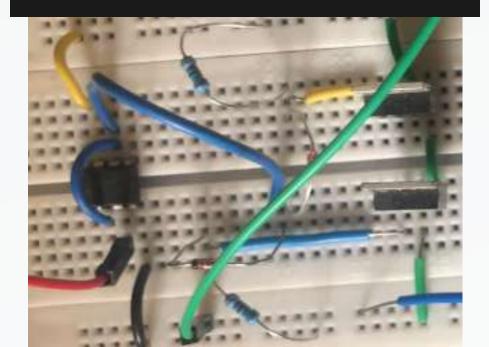

WORKING


When the input signal is in its positive half cycle, the nph transistor is on and the pnp is turned on during the negative half cycle. The small resistors in series allow for a low impedence path thus increasing the current in the power amplifier. This results in a higher power output since P=I*I*RL . Since I is larger we get a larger power output.

SIMULATION

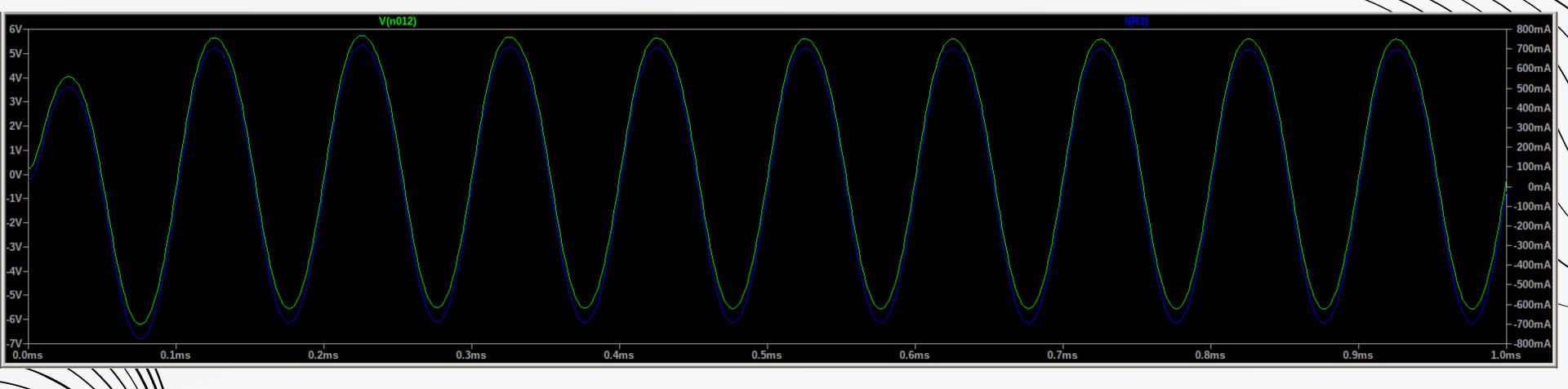


We observe that the current output has increased and the output power is more than the minimum power requirements for the speaker to run

HARDWARE OUTPUT

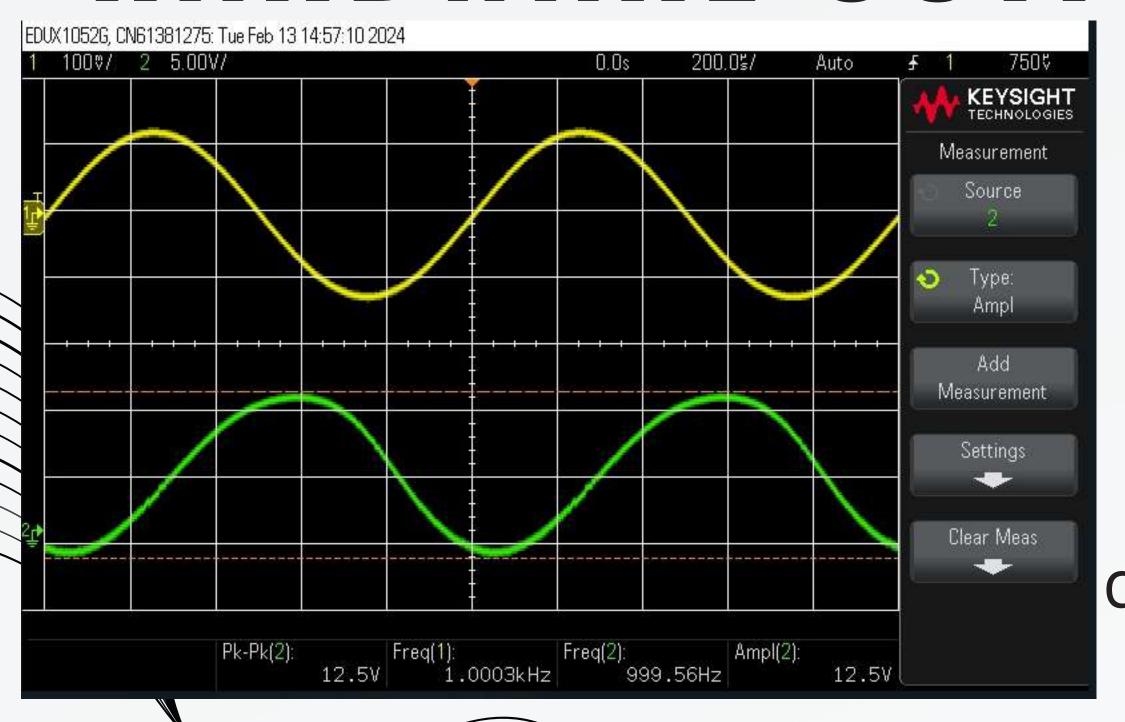


The voltage is observed to remain the same but the power output drastically increases

FINAL SIMULATIONS

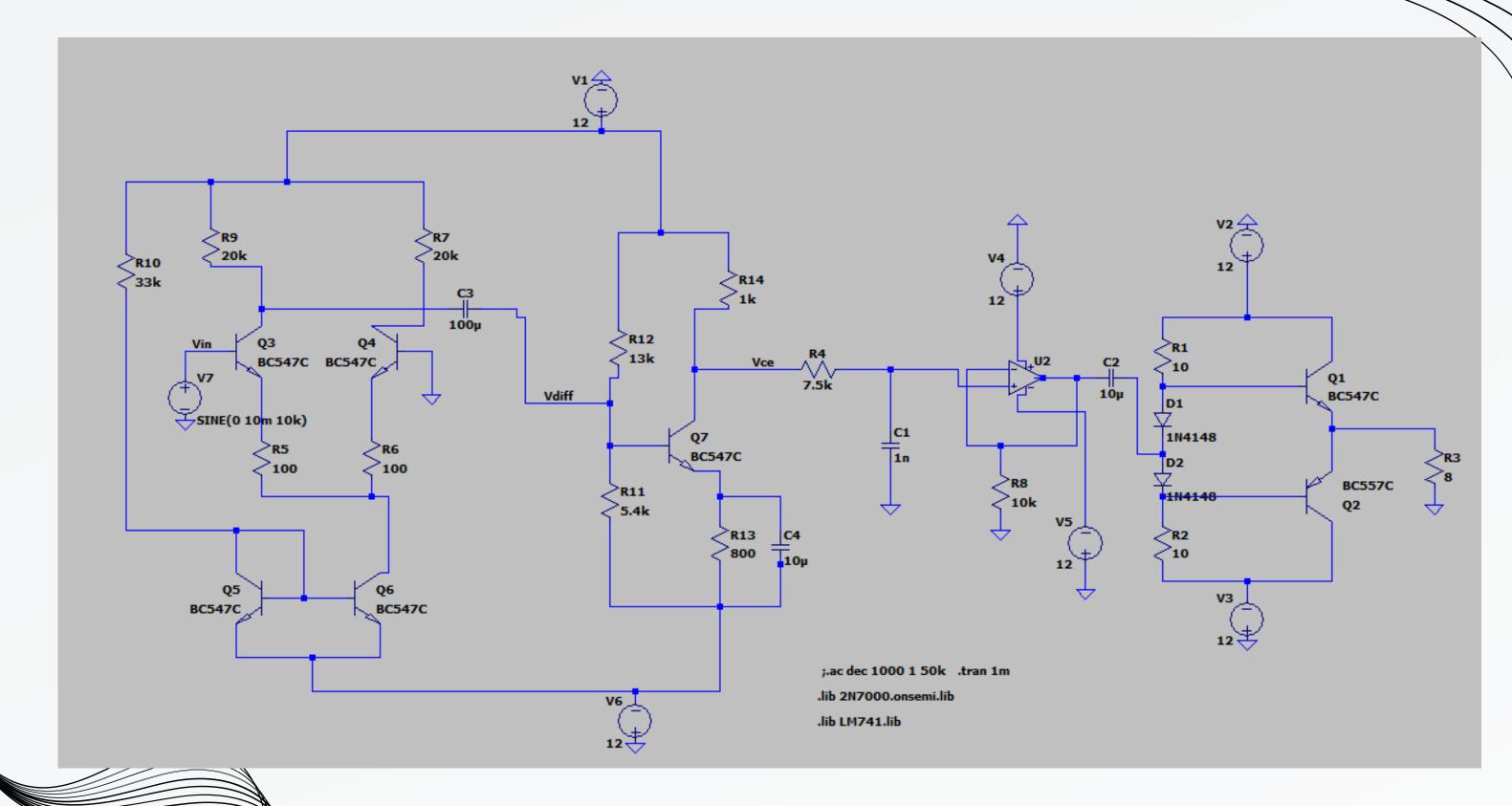


FINAL SIMULATION

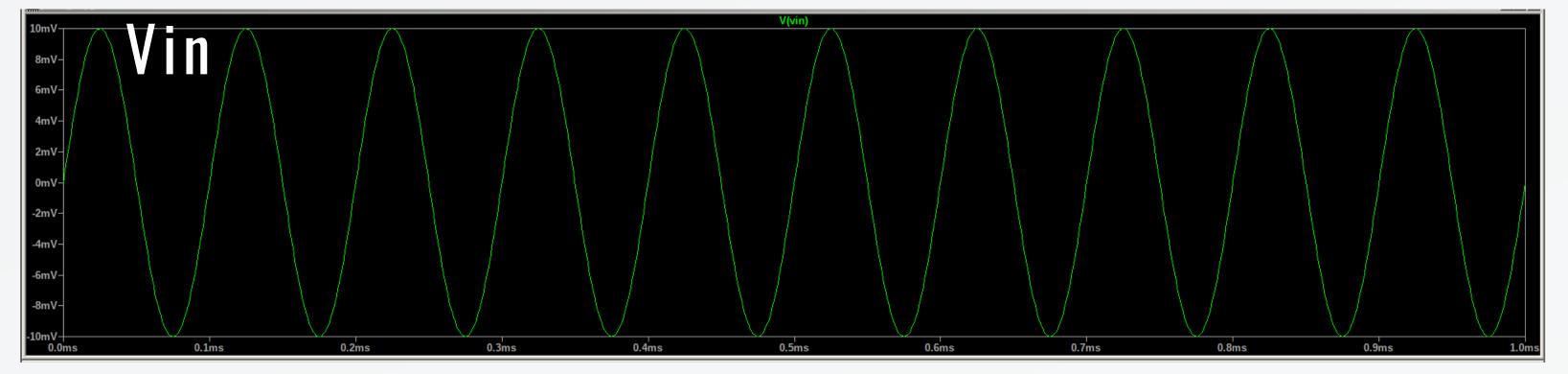Input - a sine wave of amplitude 10 mV and frequency 10kHz




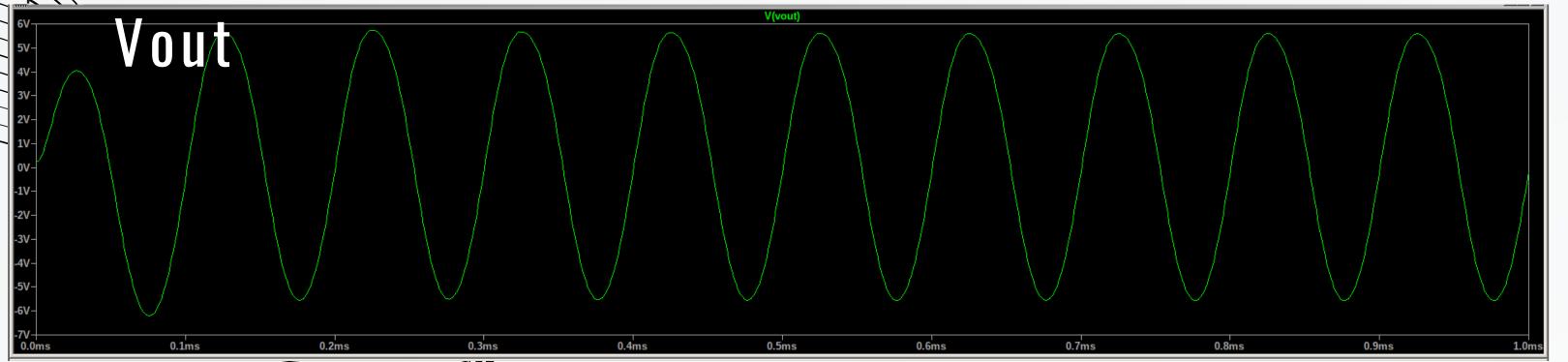Qutput- an amplified wave at 5.8 V and 10kHz with sufficient power to operate a





HARDWARE OUTPUT

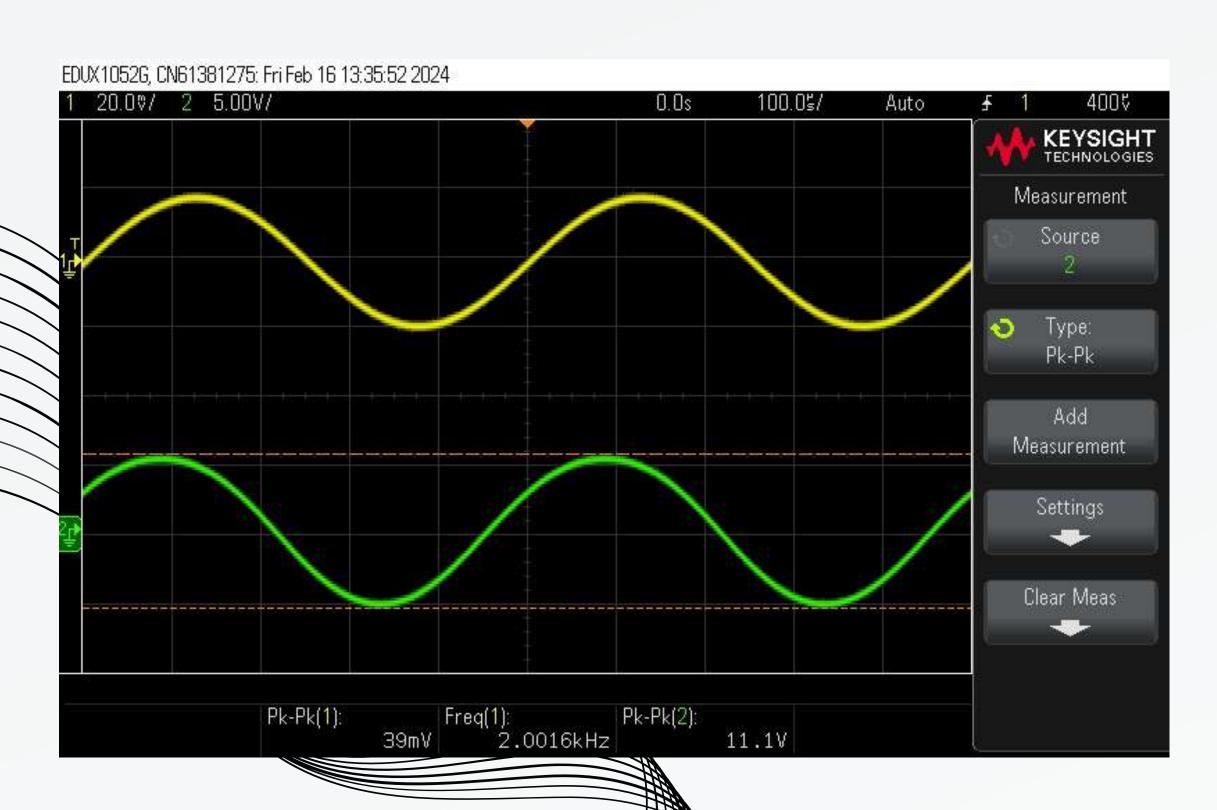

Results for 2kHz sine wave at 20 mV amplitude when it is provided as input for the designed audio amplifier. The output is an amplified wave at 11.1 V at the end of the power amplifier stage with minimal noise or distortions. Therefore, the goal of the project was achieved.

THEEND

